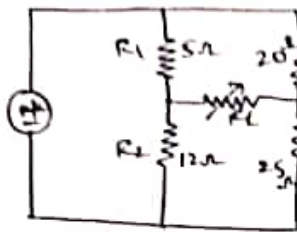


# CIRCUIT CHALLENGE (SIMULATION) [USING CIRCUIT LAB]

→ Max. power transfer

GULBI GOURI SHANKER

4AL18EC018



Disconnect the load resistance from the load terminals a and b. To represent the given circuit as Thevenin's equivalent, we are to determine the thevenin voltage  $V_{TH}$  and Thevenin's equivalent resistance  $R_{TH}$ .

The thevenin's voltage or voltage across the terminal AB is  $V_{AB} = V_A - V_B$

$$V_A = V \times R_2 / (R_1 + R_2)$$

$$= 30 \times 12 / (5 + 12)$$


$$V_A = 21.17V$$

$$V_B = V \times R_4 / (R_3 + R_4)$$


$$= 30 \times 25 / (20 + 25)$$

$$V_B = 16.66V$$
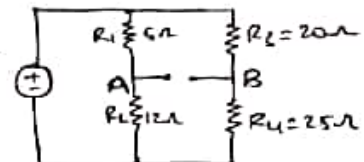
$$\therefore V_{TH} = V_{AB} = V_A - V_B = 4.51V$$



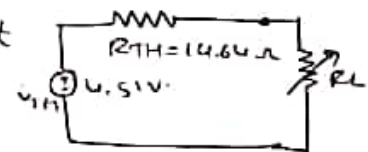
To calculate the thevenin's equivalent circuit  $R_{TH}$  by replacing source with their internal resistance.



$$R_{TH} = R_{AB} = (R_1 R_2 / (R_1 + R_2)) + (R_3 R_4 / (R_3 + R_4))$$

$$R_{TH} = 14.64\Omega$$

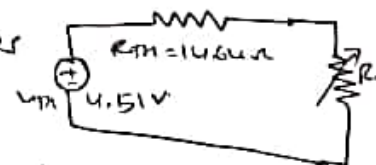By reconnecting the load resistance the thevenin equivalent circuit can be obtained as



For the maximum power transfer theorem,  $R_L$  value must be equal to  $R_{TH}$  to deliver maximum power to the load.

$$\therefore R_L = R_{TH} = 14.64\Omega$$

And the maximum power transferred to load  $R_L$  is

$$P_{max} = V_{TH}^2 / 4 R_{TH}$$

$$P_{max} = (4.51)^2 / 4 \times 14.64$$

$$P_{max} \Rightarrow 347.3 \text{ m watt.}$$

DC

P(RL) 347.3 mW

+ Add Expression

Run DC Solver

DC Sweep

Time Domain

Frequency Domain

