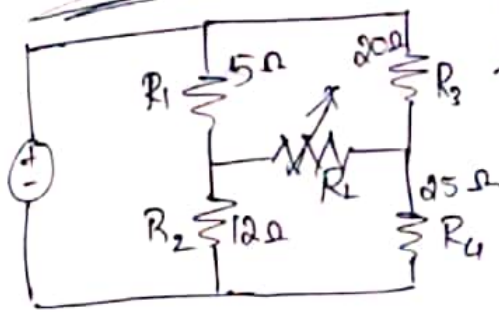


Circuit Challenge (SIMULATION) (using circuit lab)

Max. Power transfer:



Disconnect the load resistor from the load terminals a and b. To represent the given circuit as thevenin's equivalent we have to determine the

thevenin's voltage V_{th} and Thevenin's equivalent

The thevenin's voltage or voltage across the terminal AB is $V_{AB} = V_A - V_B$

$$V_A = V \times R_2 / (R_1 + R_2)$$


$$= 30 \times 12 / (5 + 12)$$

$$V_A = \underline{21.17V}$$

$$V_B = V \times R_4 / (R_3 + R_4)$$

$$= 30 \times 25 / (20 + 25)$$

$$V_B = \underline{16.66V}$$

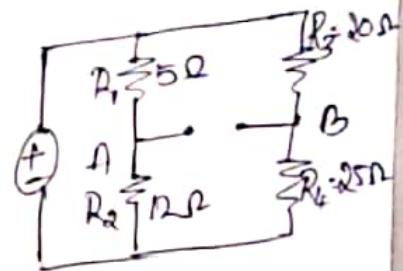

To calculate the thevenin's equivalent circuit R_{th} by replacing source with their internal resistance

$$R_{TH} = R_{AB} = (R_1 R_2 / (R_1 + R_2)) + (R_3 R_4 / (R_3 + R_4))$$

$$R_{TH} = \underline{14.64\Omega}$$

By reconnecting the load resistance the thevenin's equivalent circuit can be obtained as

For the maximum power transfer theorem, R_L value must be equal to R_{TH} to deliver maximum power to the load

$$\therefore R_L = R_{TH} = 14.64\Omega$$

And the maximum power transferred to load R_L is

$$P_{max} = V_{TH}^2 / 4 R_{TH}$$

$$P_{max} = (4.51)^2 / 4 \times 14.64 = \underline{347.3 \text{ watt}}$$

DC

V(VIN)	30.00 V	
V(VOUT)	18.38 V	
I(RLnA)	-154.0 mA	
V(RLnB)	20.63 V	
I(RLnB)	154.0 mA	

+ Add Expression

Export Results...

Run DC Solver

