

Circuit challenge [SIMULATION]


3/8/20

Date: / /

→ Max. power transfer :-

Rakshita. C.U.

HALLIBRECH2.

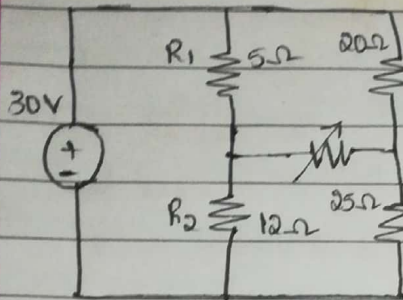

Disconnect the load resistance from the load terminals a & b. To represent the given ckt as. The Venin's equivalent we have to determine V_{th} & R_{th} .


The thevenin's voltage or voltage across the terminal AB is $V_{AB} = V_A - V_B$.

$$V_A = V \times \frac{R_2}{R_1 + R_2} = 30 \times \frac{12}{5 + 12} = 21.7V$$

$$V_B = V \times \frac{R_4}{R_3 + R_4} = 30 \times \frac{25}{20 + 25} = 16.66V$$

$$V_B = 16.66V$$
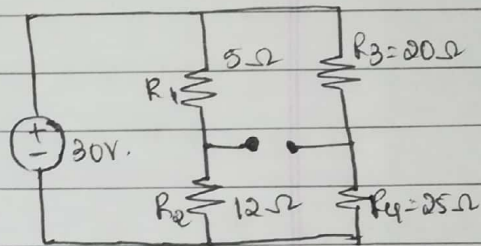
$$\therefore V_{th} = V_{AB} = V_A - V_B = 4.51V$$



- To calculate R_{th} : By replacing source with their internal resistance.

$$R_{th} = R_{AB} = \left(\frac{R_1 R_2}{R_1 + R_2} \right) + \left(\frac{R_3 R_4}{R_3 + R_4} \right)$$

$$R_{th} = 14.64 \Omega$$


$$\text{where } R_L = R_{th} = 14.64 \Omega$$

And the max. power transmitted to load R_L is

$$P_{max} = \frac{V_{th}^2}{4 R_{th}}$$

$$= \frac{(4.51)^2}{4 \times 14.64}$$

$$P_{max} = 343.3 \text{ mW}$$

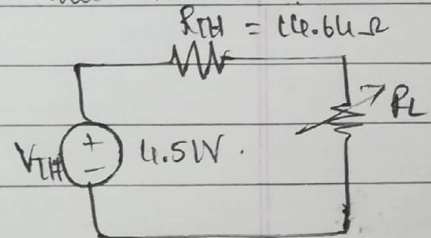

DC

P(RL)

347.3
mW

+ Add Expression

Export Results...

Run DC Solver

DC Sweep

Time Domain

Frequency Domain

