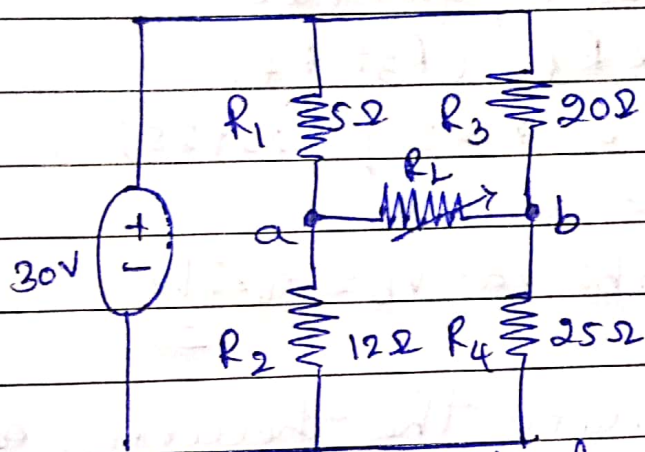



Sindhu.S

4AL18EG049

Circuit simulation for the given problem using circuit lab [Maximum power transfer]



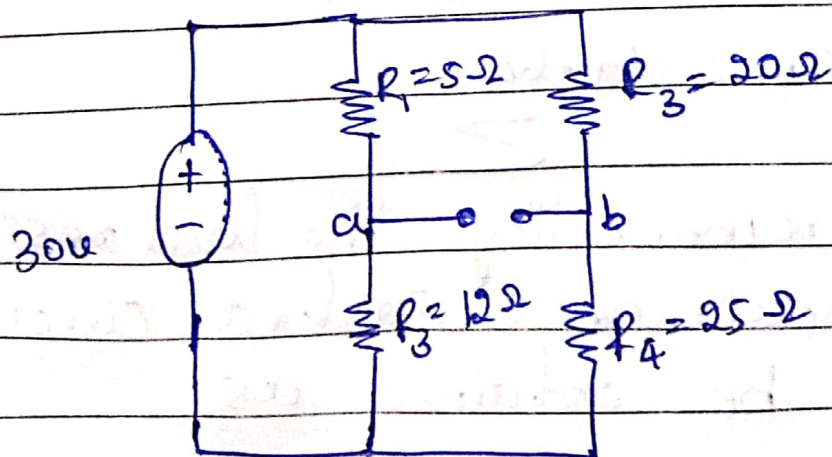Disconnect the load resistance from the load terminals a and b. To represent the given circuit as thevenin's equivalent. We are to determine the thevenin's voltage V_{th} and thevenin's equivalent resistance R_{Th} .



The Thevenin's Voltage @ Voltage across the terminals ab is $V_{ab} = V_a - V_b$

$$V_a = V_a - V_b$$

$$V_a = V \times R_2 / (R_1 + R_2)$$
$$= 30 \times 12 / (5 + 12)$$

$$V_a = 21.17 \text{ V}$$

$$V_b = V \times R_4 / (R_3 + R_4)$$
$$= 20 \times 25 / (20 + 25)$$
$$= 16.66 \text{ V}$$


$$V_{th} = V_{ab} = V_a - V_b = 4.51 \text{ V}$$

To calculate the Thevenin's equivalent resistance R_{th} by replacing source with their internal resistance (here assume that the voltage source has zero internal resistance so it becomes a short circuit).

$$R_{th} = R_{ab} = (R_1 R_2 / (R_1 + R_2)) + (R_3 R_4 / (R_3 + R_4))$$

$$R_{th} = 14.64 \Omega$$

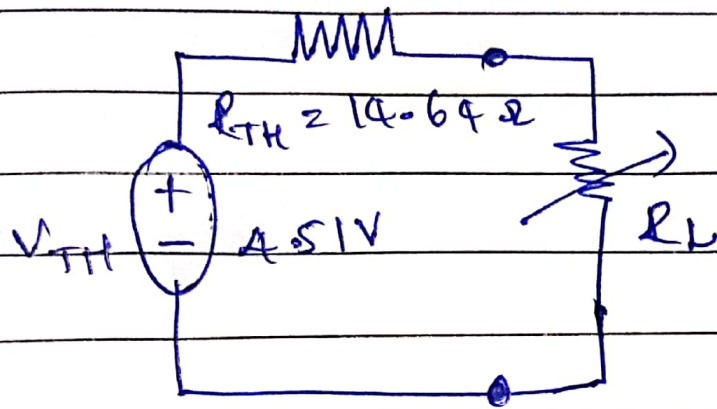By reconnecting the load resistance the Thevenin's equivalent circuit can be obtained as



for the maximum power transfer, R_L value must equal to the R_{TH} to deliver maximum to the load.

$$\therefore R_L = R_{TH} = 14.64 \Omega$$

And the maximum power transferred to load R_L i.e

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

$$P_{max} = \frac{(4.5)^2}{4 \times 14.64}$$

$$= 347.3 \text{ mWatt}$$