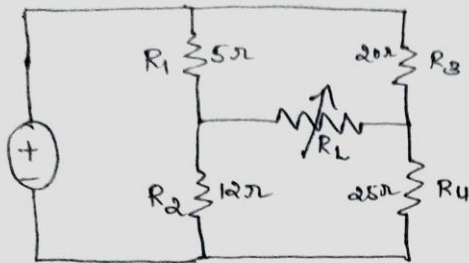


Circuit challenge

Vaishnavi M
1418EC055

Max Power transfer:



Disconnect the load resistance from the load terminals a & b. To represent the given circuit as Thvenin's Equivalent we have to determine

the Thvenin's voltage V_{TH} and Thvenin's equivalent

The Thvenin's Voltage (\odot) Voltage across the terminal AB is $V_{AB} = V_A - V_B$

$$V_A = V \times R_2 / (R_1 + R_2)$$

$$= 30 \times 12 / (5 + 12)$$


$$V_A = 21.17V$$

$$V_B = V \times R_4 / (R_3 + R_4)$$

$$= 30 \times 25 / (20 + 25)$$

$$V_B = 16.66V$$
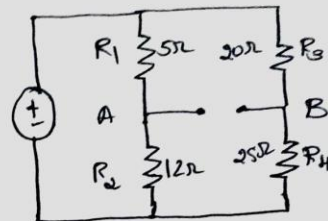
$$\therefore V_{TH} = V_{AB} = V_A - V_B = 4.51V$$




To calculate the Thvenin's equivalent circuit R_{TH} by replacing source with their internal resistance

$$R_{TH} = R_{AB} = (R_1 R_2 / (R_1 + R_2)) + (R_3 R_4 / (R_3 + R_4))$$

$$R_{TH} = 14.64\Omega$$

by reconnecting the load resistance the Thvenin's equivalent circuit can be obtained as

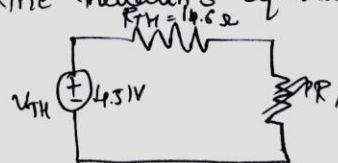For the maximum power transfer theorem, R_L value must be equal to R_{TH} to deliver maximum power to the load. $\therefore R_L = R_{TH} = 14.64\Omega$



And the maximum power transferred to load R_L is

$$P_{max} = V_{TH}^2 / 4 R_{TH}$$

$$P_{max} = (4.51)^2 / 4 \times 14.64 = 347.3 \text{ mWatt}$$

▼ DC

P(RL)

347.3
mW

+ Add Expression

Export Results...

Run DC Solver

▸ DC Sweep

▸ Time Domain

▸ Frequency Domain

