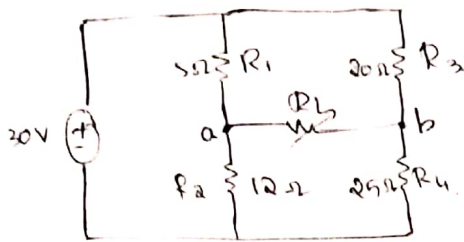



Circuit Simulation for the problem:

Sneha G
4418EC050

[Maximum power transfer]



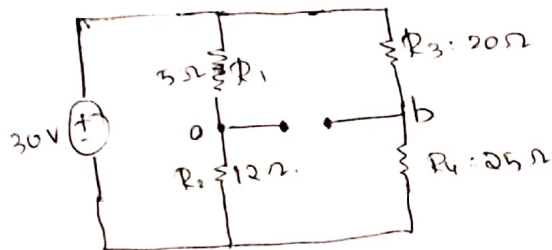Disconnect the load resistance from the load term a & b. To represent the given circuit as Thevenin's equivalent. We are to determine V_{TH} & R_{TH} .



Thevenin's voltage or voltage across the terminals ab is $V_{ab} = V_a - V_b$

$$V_a = V_a - V_b$$

$$V_a = V \times R_2 / (R_1 + R_2)$$

$$= 30 \times 12 / (5 + 12)$$

$$V_a = \underline{21.17 V}$$

$$V_b = V \times R_4 / (R_3 + R_4)$$

$$= 30 \times 25 / (20 + 25)$$

$$= \underline{16.66 V}$$


$$\therefore V_{TH} = V_{ab} = V_a - V_b = \underline{4.51 V}$$

To calculate Thevenin's equivalent resistance R_{TH} by replacing sources with internal resistance [Here assume that voltage source has zero internal resistance]

$$R_{TH} = R_{ab} = (R_1 R_2 / (R_1 + R_2)) + (R_3 R_4 / (R_3 + R_4))$$

$$R_{TH} = \underline{\underline{14.64 \Omega}}$$

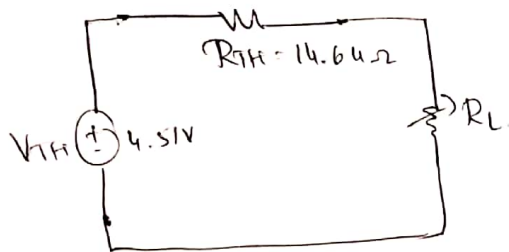By reconnecting the load resistance, the Thevenin's equivalent circuit can be obtained as



For the max. power transfer, R_L value must be equal to the R_{TH} to deliver max. power to the load.

$$\therefore R_L = R_{TH} = \underline{\underline{14.64 \Omega}}$$

And the maximum power transformed to R_L is.

$$P_{max} = V_{TH}^2 / 4R_{TH}$$

$$P_{max} = (4.51)^2 / 4 \times 14.64 \Rightarrow \underline{\underline{347.3 \text{ mWatt}}}$$

