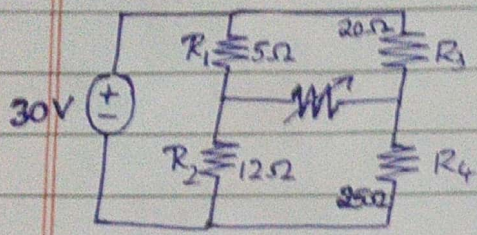


Circuit Challenge [SIMULATION]

AKSHATHA.Y.E

4ALIBEC005

→ Max. power transfer:



Disconnect the load resistance from the load terminals a & b. To represent the given ckt as Thevenin's equivalent. We have to determine V_{TH} and R_{TH} .

The Thevenin's voltage or voltage across the terminal AB is $V_{AB} = V_A - V_B$


$$V_A = V \times \frac{R_2}{(R_1 + R_2)} = 30 \times \frac{12}{(5 + 12)}$$

$$V_A = 21.7V$$

$$V_B = V \times \frac{R_4}{(R_3 + R_4)} = 30 \times \frac{25}{(20 + 25)}$$

$$V_B = 16.66V$$
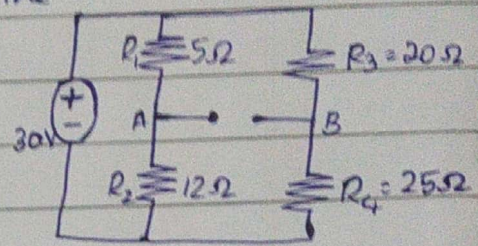
$$\therefore V_{TH} = V_{AB} = V_A - V_B = 4.51V$$



- To calculate R_{TH} : By replacing source with their internal resistance.

$$R_{TH} = R_{AB} = \left(\frac{R_1 R_2}{R_1 + R_2} \right) + \left(\frac{R_3 R_4}{R_3 + R_4} \right)$$

$$R_{TH} = 14.64\Omega$$

$$R_{TH} = 14.64\Omega$$


where $R_L = R_{TH} = 14.64\Omega$

And the max. power transmitted to load R_L is

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

$$= \frac{(4.51)^2}{4 \times 14.64}$$

$$= 343.3mW$$

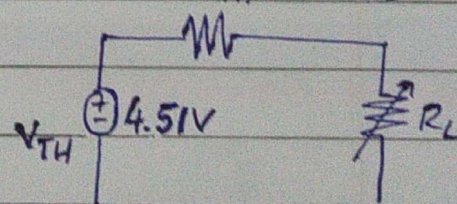

DC

P(RL) 347.3 mW

+ Add Expression

Export Results

Run DC Solver

DC Sweep

Time Domain

Frequency Domain

