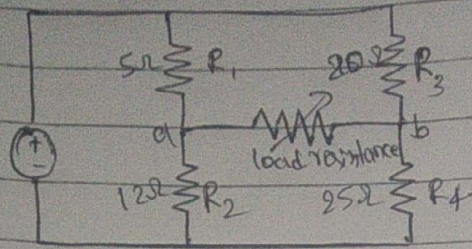


circuit challenge (simulation)



Disconnect the load resistance from the load terminals a and b. To represent the given circuit as thevenin's equivalent, we are to determine the thevenin voltage, V_{TH} and thevenin's equivalent resistance R_{TH} .

The thevenin's voltage or voltage across the terminal AB is $V_{AB} = V_A - V_B$

$$V_A = V \times R_2 / (R_1 + R_2)$$

$$= 30 \times 12 / (5 + 12)$$


$$= 21.17 \text{ V}$$

$$V_B = V \times R_4 / (R_3 + R_4)$$

$$= 30 \times 25 / (20 + 25)$$

$$= 16.66 \text{ V}$$
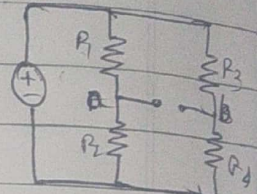
$$V_{TH} = V_{AB} = V_A - V_B = 4.51 \text{ V}$$




To calculate the thevenin's equivalent circuit R_{TH} by replacing source with their internal resistance

$$R_{TH} = R_{AB} = (R_1 R_2 / (R_1 + R_2)) + (R_3 R_4 / (R_3 + R_4))$$

$$R_{TH} = 14.64 \Omega$$

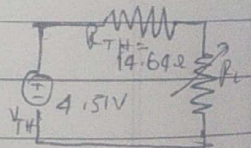By reconnecting the load resistance the thevenin's equivalent circuit can be obtained



For the maximum power transfer, R_L value must be equal to R_{TH} to deliver maximum power to the load. $\therefore R_L = R_{TH} = 14.64 \Omega$

And the maximum power transferred to load R_L is

$$P_{max} = V_{TH}^2 / 4 R_{TH}$$

$$P_{max} = (4.51)^2 / 4 \times 14.64$$

$$P_{max} = 347.3 \text{ m watt}$$

DC

P(RL) 347.3 mW

+ Add Expression

Run DC Solver

DC Sweep

Time Domain

Frequency Domain

